

Logic Design (Part 3)

Combinational Logic Devices (Chapter 3 + Notes)

Based on slides © McGraw-Hill
Additional material © 2013 Farmer
Additional material © 2020 Narahari

1

Digital Logic Circuits

- we can build the basic logic gates using transistors
- Can build **any** boolean function using these gates
 - Theory underlying design of Boolean functions ..Boolean Algebra
 - Optimize circuit using Karnaugh maps
- **Power of abstraction....To build boolean functions, you can work with basic gates – no need to go down to the transistor level !!**
- Use these gates as building blocks to build more complex combinational circuits
 - Combinational Logic Devices: Adder, Multiplier, Multiplexer, Decoder,
 - ...any boolean function

2

2

Definitions: Combinational and Sequential Logic Circuits

- A circuit is a collection of devices that are physically connected by wires
 - Combinational circuit
 - Sequential circuit
- In Combinational circuit the input determines output
- In sequential circuit, the input and the previous 'state' (previous values) determine output and next 'state'
 - Need to 'remember' previous value – need **memory** device
 - Need circuit to implement concept of storage
 - This is out next topic.....

3

3

Recall our Goal....

- Design a machine that translates from natural language to electrons running around to solve the problem
 - We now have devices (transistor) that can get electronics to run around based on input signals....and built logic gates using transistors
- Next: we want to build a computer
 - First step: Design a collection of logic devices that implement important functions that will be needed to build our computer
- S/W Analogy: When you write your software, you are using a collection of concepts, tools, IDEs and libraries
 - Each has been built, and tested, for you
 - All you have to do is combine them!

4

4

Combinational Logic Devices

- We saw how we can build the simple logic gates using transistors and build **any** boolean function using these gates
- Use these gates as building blocks to build more complex combinational circuits
 - **Decoder**: based on value of n-bit input control signal, select one of 2^N outputs
 - **Multiplexer**: based on value of N-bit input control signal, select one of 2^N inputs.
 - **Adder**: add two binary numbers
 - ...any boolean function
- **SW Analogy: We are building a library of functions**
 - To design your solution, you can use any device in the library!

5

5

Three Devices we focus on...

- N-bit Adder
 - Can build Subtract using Adder
- Decoder
 - Decode a bit string
- Multiplexer
 - A channel selector
- Other useful combinational logic devices
 - Multipliers
 - Shifters (but may need storage)
 - Comparators (to compare two numbers)
 - ...

6

6

1. N-bit Adder

- Add two N-bit numbers, represented in 2's complement
- Algorithm (for now): add corresponding bit positions, starting with least significant position, and propagate the carry bit leftward.
 - In practice: there are faster algorithms
 - Big-Oh Analysis:
 - To add N bit numbers how 'far' will the carry propagate ?

7

7

Binary Addition

- Binary addition – just like base 10 (decimal) !
 - Add from right to left, propagating carry
 - Example using unsigned integers

$$\begin{array}{r}
 10010 \text{ (18)} \\
 + 01001 \text{ (9)} \\
 \hline
 11011 \text{ (27)}
 \end{array}
 \qquad
 \begin{array}{r}
 10010 \text{ (18)} \\
 + 01011 \text{ (11)} \\
 \hline
 11101 \text{ (29)}
 \end{array}
 \qquad
 \begin{array}{r}
 01111 \text{ (15)} \\
 + 00001 \text{ (1)} \\
 \hline
 10000 \text{ (16)}
 \end{array}$$

carry (curved arrow from bit 1 to bit 2 in the second example)
 (curved arrows from bit 1 to bit 2, bit 2 to bit 3, bit 3 to bit 4 in the third example)

Key Observation: We add one bit at a time
 therefore, building block is a 1-bit adder
Use 1-bit adder to build N-bit adder!

8

8

1-bit Adder

- Two inputs A, B and Two outputs: S (sum) and Carry out (C)
- Truth table:
- Problem?
- This works only for bit 0 where there is no Carry-in
 - Called a half adder
- In general, we can have a carry-in input, so 3 inputs are A, B, C_{in} (carry-in) and 2 outputs S, C_{out} (carry out)

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


9

9

Binary Arithmetic: Half Adder

- Logical Function: **Half Adder**, implement Carry Out:

A	B	Sum	C _{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

Half Adder's Logic Function:

$$\text{SUM} = ((A' \text{ AND } B') \text{ OR } (A \text{ AND } B))'$$

$$\text{C} = ((A' \text{ AND } B') \text{ OR } (A' \text{ AND } B) \text{ OR } (A \text{ AND } B'))'$$



Realize though: C = (A AND B), this isn't always best way!

10



10

Addition: Full Adders

  - There is a limit with the half adder
 - It can't implement multiple-bit addition



  - It works for "least significant bit," but won't work for the next




- We need an adder that has 3 inputs and 2 outputs

3-11

11

11

Full Adder

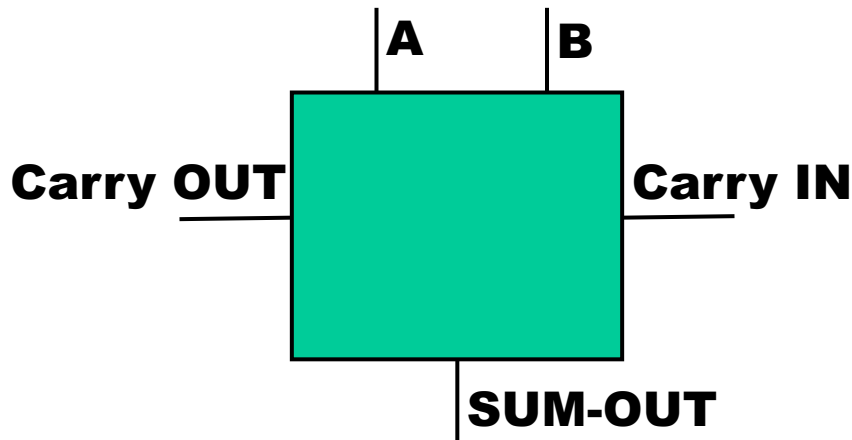

12

12

Truth Table for Full-Adder


A	B	Carry In	Out	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

13

13

1-bit Full Adder

 ▪ Add two bits and carry-in, produce one-bit sum and carry-out.





A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

14

14

N-bit Adder

  

CarryOut: useful for detecting overflow


CarryIn: assumed to be zero if not present

3-15

15

15

Four-bit Adder

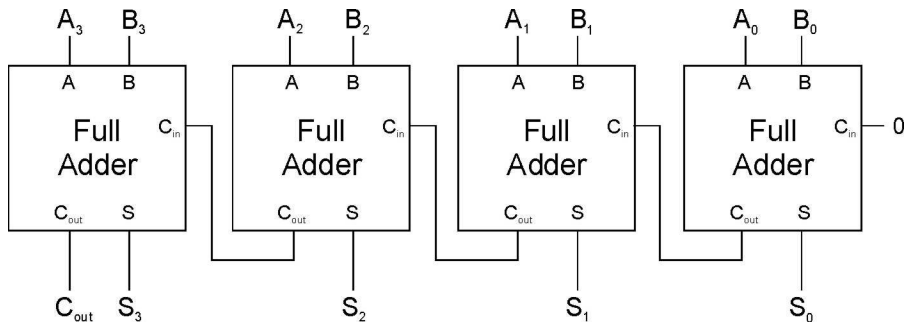


16

16

How about a “subtractor?”

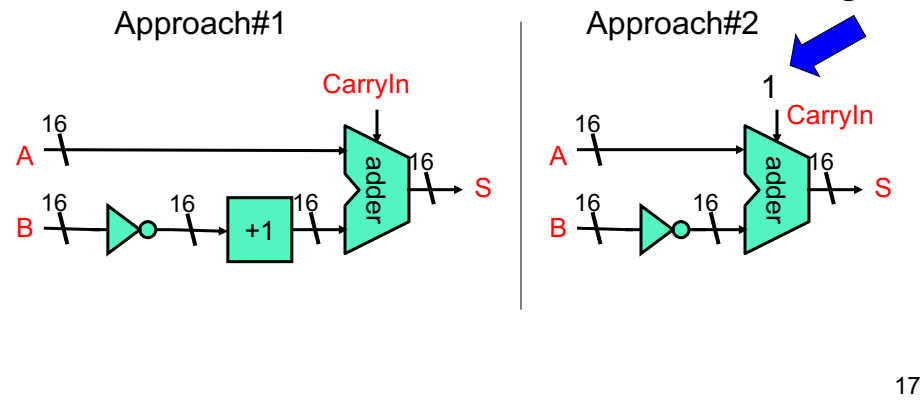- Build a subtractor from out multi-bit adder
 - Calculate $A - B = A + -B$
 - Negate B
 - Recall $-B = \text{NOT}(B) + 1$



17

The Decoder

- Useful for recognizing a particular bit pattern of 0's and 1's
- Connection to Computer Organization:
 - Program consists of instructions -- coded in binary (0's and 1's)
 - We want to look at a bit string for the instruction and determine what the instruction is
 - Is it an ADD or a MULT or a GOTO or.....
 - each instruction is given a unique encoding & decoder looks at the encoding and determines which ONE of the instructions the code corresponds to (i.e, which instruction has to be executed)
- In S/W, a “case”/switch statement:
 - One of the cases will be evaluated depending on value of 'input'

18

18

Switch (case) statement in C

```
int x;
...
switch(x) {
    case 0: /* if x=0 call func Kevin */
        Kevin(); /* ex: Kevin does add */
        break;
    case 1: /* if x=1 call func Graham */
        Graham();
        break;
    case 2: /* if x=2 call func Sarah */
        Sarah(); /* ex: Sarah does AND */
        break;
    case 3: /* if x=3 call func Linnea */
        Linnea();
        break;
    default: printf("invalid value of x\n");
             break;
}
..
```


19

19

N-2^N Decoder

- N inputs – these represent the binary encoding of the 2^N Outputs
 - Ex: if N=2, then 4 outputs 0,1,2,3, encoded to be 'switched on' when inputs are one of 00, 01, 10, 11 respectively

- Schematic:

 

Notational Convenience: Typically we label the outputs from 0 to 2^N-1: x_0, x_1, \dots, x_{N-1}
Output $x_i = 1$ if decimal value of input = i

20

20

Designing a Decoder: Truth table 4 output lines x_0, x_1, x_2, x_3 & 2 inputs a_1, a_0

From truth table, design circuit:


$$x_0 = a_1' \cdot a_0' \text{ (i.e., (NOT } a_1) \text{ AND (NOT } a_0))}$$

$$x_1 = a_1' \cdot a_0 \quad x_2 = a_1 \cdot a_0' \quad x_3 = a_1 \cdot a_0$$

a_1	a_0	x_0	x_1	x_2	x_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

21

Decoder

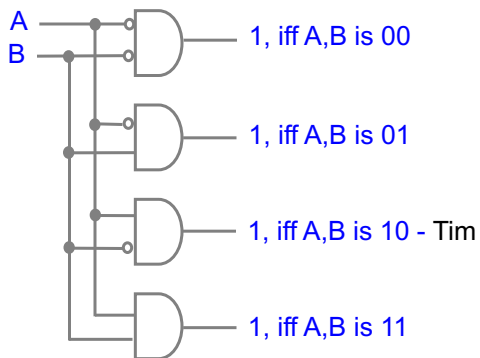

**2-bit decoder
(4 input decoder)**


- An n input decoder has 2^n outputs.
- Output i is 1 iff the binary value of the n -bit input is i .
- At any time, exactly one output is 1, all others are 0.

22

22

The Multiplexer - selector

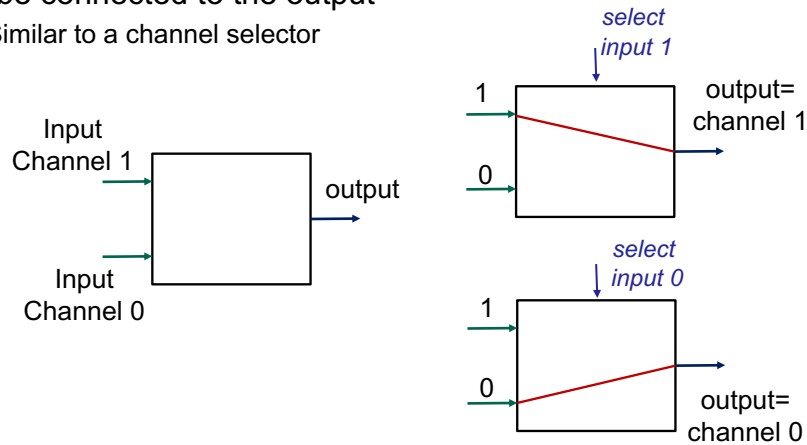- Multiplexer (MUX) is a device that selects one of the inputs to be connected to the output
 - Similar to a channel selector




This is a 2-1 Multiplexer: Selects one of 2 inputs as the output 23


23

N-1 Multiplexer

 - Multiplexer selects one of the N inputs as the output
 - It needs $\log_2 N$ 'select lines' to determine which of the N inputs is selected to appear at the output
 - Schematic of a MUX:



 - Multi-bit muxes
 - Can switch an entire "bus" or group of signals
 - Switch n-bits with n muxes with the same select bits
 - Built using 16 1-bit 4-1 MUXes and has same S



24



24

The Multiplexer (MUX) – 2-1 and 4-1 MUX

- Selector/Chooser of signals – *Imagine Switching Railroad Tracks*


- Multi-way switch

2-to-1 Mux

  

Input "S" selects A or B to attach to "O" output
Acts like an "IF/ELSE" statement

4-to-1 Mux

 


3-25

25

25


Designing 4-1 MUX Using Logic Gates

Multiplexer (MUX)

 

- In general, a MUX has
 - 2^n data inputs
 - n select (or control) lines
 - and 1 output.
- It behaves like a channel selector.
 
$$\text{Out} = A \cdot \bar{S}_0 \cdot \bar{S}_1 + B \cdot \bar{S}_0 \cdot S_1 + C \cdot S_0 \cdot \bar{S}_1 + D \cdot S_0 \cdot S_1$$



A 4-to-1 MUX:

Out takes the value of A, B, C or D
depending on the value of S (00, 01, 10, 11)


Out = A if S=00 Out = B if S = 01

Out = C if S=10 Out=D if S=11

27

 Example: MUX in a circuit

- Inputs A, B, C and x (select signal); Output F
- Devices/Gates: 2-1 MUX, AND gate



- If $x=0$, output of MUX = B and $F = B.C$
- If $x=1$, output of MUX = A and $F = A.C$
- Can write $F = xAC + x'BC$

28

28

Combinational vs. Sequential

▪ Combinational Circuit

- always gives the same output for a given set of inputs
 - ex: adder always generates sum and carry, regardless of previous inputs

▪ Sequential Circuit

- stores information
- output depends on stored information (state) plus input
 - so a given input might produce different outputs, depending on the stored information
- useful for building “memory” elements and “state machines”

29

29

Next . . Circuits with “memory”

- First we need to build a device that can store a bit
 - Using our current ‘library’ of gates
 - Building memory follows
- How to model sequential circuits/machines
 - Methodology for designing these machines: **Finite state machine**
 - Model as a directed graph
- How to we “synchronize” and ”coordinate” the different pieces in the circuit....enter the **CLOCK**
- can we use a sequential circuit to “control” how computations take place in a processor ?
- Is a sequential circuit = Computer ?
 - Limitations of sequential machines..more in Foundations course

30



30

Appendix

31

31

  Adder/Subtractor - Approach #2 (Optimize HW)



34

34